

1. Write Up

While concept of moore and mealy machine was introduced by Dr.Dworak earlier, seeing its implementation on the FPGA board and confirming the simulation clarified a lot of questions I had.

2. Source Code (moore.v, moore_top.v, mealy.v, mealy_top.v)

Moore.v

```
module moore (  
    input wire clk,  
    input wire rst,  
    output wire [2:0] out  
);  
reg [2:0] state;  
parameter S0=3'b000, S1=3'b001, S2=3'b010, S3=3'b011, S4=3'b100,  
S5=3'b101, S6=3'b110, S7=3'b111;  
always @(posedge clk or posedge rst)  
    if(rst == 1)  
        state <= S0;  
    else  
        case(state)  
            S0: state <= S4;  
            S4: state <= S7;  
            S7: state <= S3;  
            S3: state <= S5;  
            S5: state <= S0;  
        endcase  
        assign out = state;  
endmodule
```

Moore_top.v

```
module moore_top (  
    input wire mclk,  
    input wire [0:0] btn,  
    output wire [2:0] ld  
);
```

```
moore U1(  
    .clk(mclk),  
    .rst(btn[0]),  
    .out(ld[2:0])  
);
```

```
endmodule
```

Mealy.v

```
module mealy (  
    input wire clk,  
    input wire rst,  
    input wire cin,  
    output wire out,  
    output wire [3:0] state  
);  
reg [3:0] currState, nextState;  
reg cout;  
parameter A=4'b0001, B=4'b0010, C=4'b0100, D=4'b1000;  
always @(posedge clk or posedge rst)  
    if(rst == 1)  
        currState <= A;  
    else  
        currState <= nextState;  
always @(currState or cin)
```

```
if(cin == 1)

    case(currState)

        A:

            begin

                nextState <= A;

                cout <= 1;

            end

        B:

            begin

                nextState <= D;

                cout <= 0;

            end

        C:

            begin

                nextState <= B;

                cout <= 0;

            end

        D:

            begin

                nextState <= C;

                cout <= 1;

            end

    endcase

else

    case(currState)

        A:

            begin

                nextState <= B;

                cout <= 0;

            end
```

```

        B:
        begin
            nextState <= C;
            cout <= 1;
        end

        C:
        begin
            nextState <= A;
            cout <= 1;
        end

        D:
        begin
            nextState <= D;
            cout <= 0;
        end
    endcase

    assign state = currState;

    assign out = cout;

endmodule

Mealy_top.v

module mealy_top (
    input wire mclk,
    input wire [0:0] sw,
    input wire [0:0] btn,
    output wire [4:0] ld
);

```

```

mealy U1 (
    .clk(mclk),
    .rst(btn[0]),
    .cin(sw[0]),
    .state(ld[3:0]),
    .out(ld[4])


);

endmodule


```

3. Simulation (moore, mealy)

Moore

 

Mealy

 

4. Demo Code

Demo-Code (moore) :

Demo-Code (mealy) :