

1. Write Up & Prelab Code

In this lab I've learnt how to alter the parameters of code I already know to solve a new problem. Learning to change to clk inputs enhanced my understanding of what each command does. Drawing out the k-map from 7segment decoder was good exercise, but I wish we'd gone a bit more into the ways different columns interact. The logic functions from K-map helped me visualize where the Verilog code came from.

Prelab-Code: 8830

2. Source Code (hex7seg.v, hex7seg_top.v, mux7seg.v, x7seg.v, x7seg_top.v, clkdiv.v, counter.v)

Hex7seg.v

```
module hex7seg (  
    input wire [3:0] x ,  
    output reg [6:0] a_to_g  
);  
always @(*)  
case(x)  
0: a_to_g = 7'b0000001;  
1: a_to_g = 7'b1001111;  
2: a_to_g = 7'b0010010;  
3: a_to_g = 7'b0000110;  
4: a_to_g = 7'b1001100;  
5: a_to_g = 7'b0100100;  
6: a_to_g = 7'b0100000;  
7: a_to_g = 7'b0001111;  
8: a_to_g = 7'b0000000;  
9: a_to_g = 7'b0000100;  
'hA: a_to_g = 7'b0001000;  
'hb: a_to_g = 7'b1100000;
```

```

'hC: a_to_g = 7'b0110001;
'hd: a_to_g = 7'b1000010;
'hE: a_to_g = 7'b0110000;
'hF: a_to_g = 7'b0111000;
default: a_to_g = 7'b0000001; // 0
endcase
endmodule

```

Hex7seg_top

```

module hex7seg_top (
input wire [3:0] sw ,
output wire [6:0] a_to_g ,
output wire [3:0] an ,
output wire dp
);
assign an = 4'b0000; // all digits on
assign dp = 1; // dp off
hex7seg D4 (.x(sw),
.a_to_g(a_to_g)
);
endmodule

```

MUX44

```

module mux44 (
input wire [15:0] x ,
input wire [1:0] s ,
output reg [3:0] z
);
always @(*)
case(s)
0: z = x[3:0];
1: z = x[7:4];

```

2: z = x[11:8];

3: z = x[15:12];

default: z = x[3:0];

endcase

endmodule

X7seg

module x7seg (

input wire cclk,

input wire clr,

input wire [15:0] x,

output wire [6:0] a_to_g,

output wire [3:0] an

);

wire nq0;

wire nq1;

wire [3:0] digit;

wire [1:0] q;

assign nq1 = ~(q[1]);

assign nq0 = ~(q[0]);

assign an[0] = q[0] | q[1];

assign an[1] = nq0 | q[1];

assign an[2] = q[0] | nq1;

assign an[3] = nq0 | nq1;

hex7seg U1

(.a_to_g(a_to_g),.x(digit));

mux44 U2

(.s({q[1:0]}),.x(x),.z(digit));

counter

```

#( .N(2)) U3
( .clk(cclk),.clr(clr),.q(q[1:0]));
endmodule

```

X7seg_top

```

module x7seg_top (
input wire mclk,
input wire [3:3] btn,
output wire dp,
output wire [6:0] a_to_g,
output wire [3:0] an
);
wire clk190;
wire [15:0] x;
assign x = 'hC5E;
assign dp = 1;
clkdiv U1
( .clk3(clk3),
.clr(btn[3]),
.clk(mclk)
);
x7seg U3
( .a_to_g(a_to_g),
.an(an),
.cclk(clk3),
.clr(btn[3]),
.x(x)
);
endmodule

```

Clkdiv

```

module clkdiv (

```

```

input wire clk ,
input wire clr ,
output wire clk190 ,
output wire clk25 ,
output wire clk3
);
reg [23:0] q;
// 24-bit counter
always @(posedge clk or posedge clr)
begin
if(clr == 1)
q <= 0;
else
q <= q + 1;
end
assign clk190 = q[17]; // 190 Hz
assign clk25 = q[0]; // 25 MHz
assign clk3 = q[1]; // 3 Hz
endmodule

```

Counter

```

module counter
#(parameter N = 8)
(input wire clr ,
input wire clk ,
output reg [N-1:0] q
);
// N-bit counter
always @(posedge clk or posedge clr)
begin
if(clr == 1)

```

```
q <= 0;

else


q <= q + 1;

end


endmodule
```

3. Simulation (Example 9, Example 10)

Example 9

 

Example 10

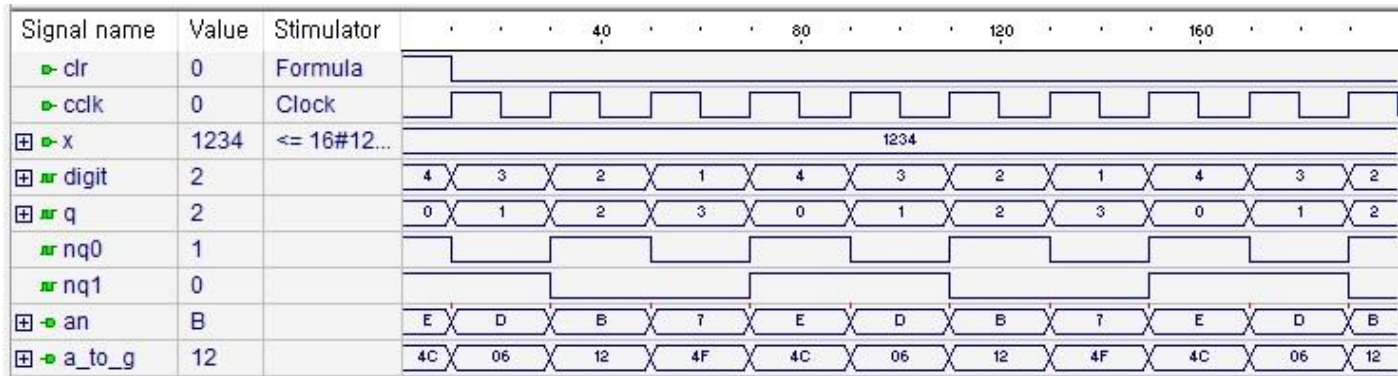

4. Demo Code

Demo9-Code: 2432

Demo10-Code: 2373