

### 1. Write Up & Prelab Code

In the prelab I've practiced how to effectively convert a logic diagram to Verilog assign statements. In the process I discovered that even without the strict grouping (ex:  $(a \wedge b) \wedge \text{cin}$ ), the simulation still worked fine. However in spirit of making the implicit explicit I followed the diagram exactly. In fixing 4-bit adder code from the lab book, I was able to better understand the bit adders for the demo and top level design was less abstract then k-maps.

Prelab-Code: 3297

### 2. Source Code (fulladd.v, fulladd2.v, adder4.v, adder4\_top.v)

#### Fulladd.v

```
module fulladd (  
    input wire a,  
    input wire b,  
    input wire cin,  
    output cout,  
    output wire s  
);  
  
assign s = (a ^ b) ^ cin;  
assign cout = (a&b) | ((a^b) & cin);  
endmodule
```

#### Fulladd\_top.v

```
module fulladd_top (  
    input wire [2:0] sw,  
    input wire [0:0] btn,
```

```

output wire [1:0] ld
);
fulladd U1
(
.a(sw[0]),
.b(sw[1]),
.cin(btn[0]),
.s(ld[0]),
.cout(ld[1])
);
endmodule

```

adder4.v

```

module adder4 (
input wire cin,
input wire [3:0] a,
input wire [3:0] b,
output wire cout,
output wire [3:0] s
);

```

```

wire c1;
wire c2;
wire c3;

```

```

fulladd U1
( .a(a[3]),
.b(b[3]),
.cin(c3),
.cout(cout),
.s(s[3])

```

```

);

fulladd U2
( .a(a[2]),
  .b(b[2]),
  .cin(c2),
  .cout(c3),
  .s(s[2])
);

fulladd U3
( .a(a[1]),
  .b(b[1]),
  .cin(c1),
  .cout(c2),
  .s(s[1])
);

fulladd U4
( .a(a[0]),
  .b(b[0]),
  .cin(cin),
  .cout(c1),
  .s(s[0])
);

endmodule

```

adder4\_top.v

```

module adder4_top (
  input wire [7:0] sw,
  input wire [0:0] btn,
  output wire [4:0] ld
);

```

```

wire [3:0] sum;

adder4 U1

(

.cin(btn[0]),

.a(sw[7:4]),

.b(sw[3:0]),

.cout(ld[4]),

.s(ld[3:0])


);

endmodule


```

### 3. Simulation (Example 12, Example 13)

Example 12

 

Example 13

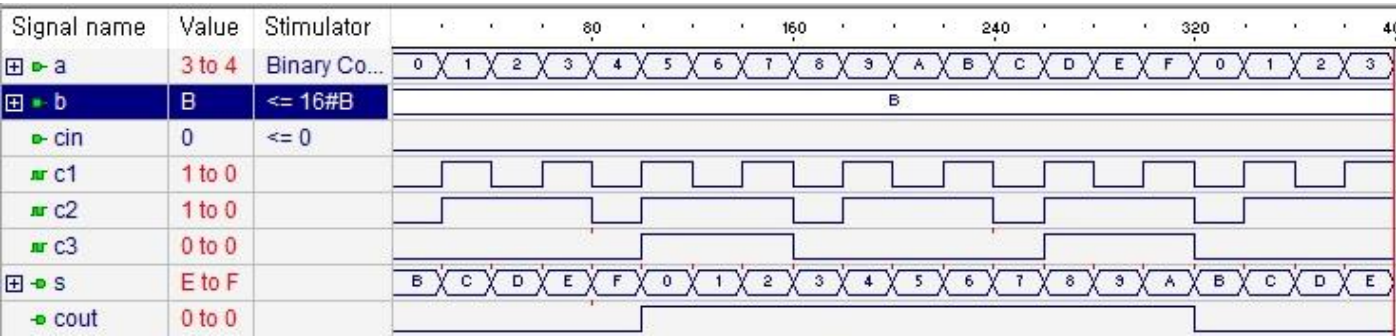

### 4. Demo Code

Demo12-Code: 6879

Demo13-Code: 1765