

1. Write Up

I chose to implement the logic function 4-1 MUX, because I felt that from example 7, this was the best explained the behavior of this mux at varying inputs. I learnt how to alter the given top level Verilog code to work according to the designed input.

2. Source Code (mux41.v, counter.v, clkdiv.v, count8_top.v)

//: 4-to-1 MUX using logic equation

```
module mux41b (  
    input wire [3:0] c ,  
    input wire [1:0] s ,  
    output wire z  
);  
    assign z = ~s[1] & ~s[0] & c[0]  
    | ~s[1] & s[0] & c[1]  
    | s[1] & ~s[0] & c[2]  
    | s[1] & s[0] & c[3];  
endmodule
```

//Counter.v

```
module counter  
#(parameter N = 8)  
(input wire clr ,  
    input wire clk ,  
    output reg [N-1:0] q  
);  
    // N-bit counter  
    always @(posedge clk or posedge clr)
```

```
begin
if(clr == 1)
q <= 0;
else
q <= q + 1;
end
endmodule
```

```
//clock divider
module clkdiv (
input wire clk ,
input wire clr ,
output wire clk190 ,
output wire clk25 ,
output wire clk3
);
reg [23:0] q;
// 24-bit counter
always @(posedge clk or posedge clr)
begin
if(clr == 1)
q <= 0;
else
q <= q + 1;
end
assign clk190 = q[17]; // 190 Hz
assign clk25 = q[0]; // 25 MHz
assign clk3 = q[0]; // 3 Hz
endmodule
```

```
// count8_top

module count8_top (

input wire mclk,

input wire [3:3] btn,

output wire [7:0] ld

);

wire clk3;

clkdiv U1

( .clk3(clk3),

.clr(btn[3]),

.clk(mclk)

);

counter

#( .N(8))

U2

( .clk(clk3),

.clr(btn[3]),


.q(ld[7:0])

);


Endmodule
```

3. Simulation (mux41, counter)

MUX41

 

Counter

 

4. Demo & Prelab Code

Demo-Code: 5853

Prelab-Code: 4585